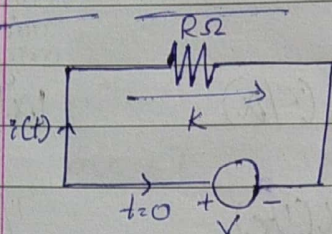


- Evaluation of initial and final conditions in RL, RC and R-L-C circuits.

→ Resistor circuit element:



At time $t=0$, $i(t) = (V/R)$ Amps.


At time $t=\infty$, $i(t) = (V/R)$ Amps.

$$i(t) = i(\infty) + [i(0) - i(\infty)] \times e^{-(t/\tau)}$$

$$i(t) = V/R + [V/R - V/R] \times e^{-(t/\tau)}$$

It confirms that, current in the resistor will follow Ohm's law.

→ Inductance circuit element:

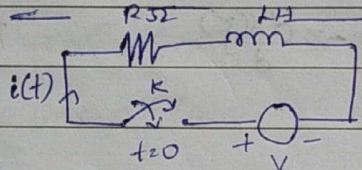

$$V_L = L \times di/dt \text{ \& hence, } L = V/i \times (di/dt)$$

So inductance property opposes the change in current.

At time $t=0$, $i(t) = 0$ Amps.

At time $t=\infty$, $i(t) = V/R$ Amps.


$$i(t) = i(\infty) + [i(0) - i(\infty)] \times e^{-(t/\tau)}$$

$$i(t) = V/R + [0 - V/R] \times e^{-(t/\tau)}$$

$$i(t) = V/R (1 - e^{-(t/\tau)})$$

inductor
opposes the
change in
current

• Capacitor circuit element:

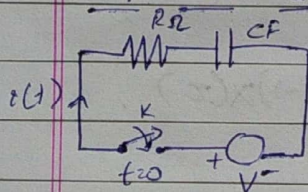

$$i_c = C \times dv_c/dt$$

$$C = i_c / (dv_c/dt)$$

So, capacitance opposes the change in voltage across it.

Switch (K) is open, and it is open for infinite time before closing.

So, capacitor is uncharged, Hence,

$V_c(0) = 0$, therefore, $V_c(0+) = 0$. So, entire applied voltage V appears across it.

- Procedure for evaluating initial & final conditions.

There is no unique procedure that must be followed in solving for initial and final conditions.


- **Initial Condition:** while solving for the initial conditions when certain circuit is switched at say, $t=0$;

If the initial condition that is, voltage across the capacitor and the current through the inductance before switching, are given in the problem statement, that is fine.

- **Final Condition:** while solving for the Final conditions when certain circuit is switched at, $t=\infty$;

- **Two Port network:**

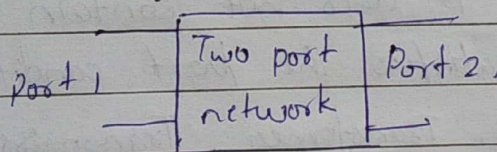It is the electrical circuit which contains the two ports but about port is a pair of terminals which connects the circuit or n/w to the external circuit.




Port condition: If the current I enters to the one terminal of the port then the same current shd leave to the other port.

If the electrical ckt or n/w contains the one such port then it is called as one port network.

Ex: of 1 port n/w: R, C, L .


Two port network: which contains 2 ports called two port network:

Eg: T-network :

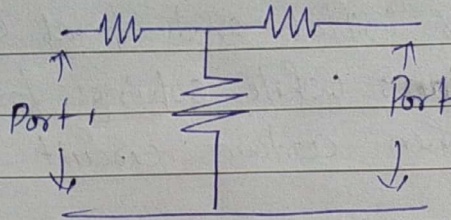

→ If it has more than 2 n/w then it is called as multiport n/w:

Eg: Directional Coupler, Circulator.

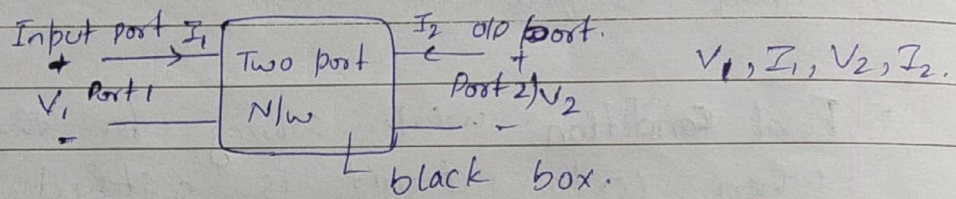

Here two port network it is used in mathematical circuit analysis for complex circuits. We can isolate the portion of larger circuits. It reduces the complexity of the circuits.

In general Any linear circuit with two pair of terminals can be regarded as two-port n/w provided that it does not contain independent source and satisfies the port condition.

Where Filters, Transformer, Transmission Line and small signal model of transistor are small example of circuit analysis.

Here for 4 variables 2 are independent variables and other 2 are dependent variables it can be expressed as

$$V_1 = f(I_1, I_2)$$

$$V_2 = f(I_1, I_2)$$

And the parameters would be described about the variables.

Two port Parameters:

① Z-Parameter:

② Y-Parameter:

③ h-Parameter:

④ ABCD or Transmission-Parameter:

⑤ Inverse Hybrid - Parameter:

⑥ Inverse Transmission-Parameter:

Python:

Application-9 Build a web-based Financial Graphs

① web based Financial Graph-

We will learn how to get stock market data loss. in terms of python.

We use Boleh library to visualize the stock market data. and even Panda also.

② Downloading Datasets with Python:
Pandas Datareader.

→ Instal this library and jupyter notebook and create jupyter file called stock analysis.

→ Data will taken from Yahoo, Finance etc. and pandas in a library.
from pandas-datareader, import data.
data. DataReader?

To get data from the source like Yahoo! we have to pass parameter.
data. DataReader(name="AAPL", data-source="yahoo", start=end=)

then save the product in a variable.
then the stock market with appear.

Stock Market Data:

→ we can minimize the data to 10 days or any number of days of stock market.

open - means open share for the share in sources like Google, Yahoo etc.

- Stock Market Data Candlestick charts.

Open, High, Low, Close, Volume and Adj Close are the needed for the Candle chart.

→ Here we build the Candlestick chart. candle chart resembles the table and data been there.

Here in candlestick chart we have to select the leaves like rectangle or line called segment.

- Candlestick charts with Bokerh Quadrants.
- Candlestick charts with bokerh Rectangles.
- Candlestick segments.
- Styling the chart.
- The concept behind Embeddy boketi chart.
- we can visualize by colouring the data.
- Embeddy the Bokerh Chart in a webpage.
First download the flask files.
- Deploying the chart website to a live Server:
Here we can access the chart.