

• Network theory - DAY 02

→ Introduction to Network theorems:

Akshatha.V.E
4ALIBEC005

These are 9 theorems in N/w theorems.


- **Linearity Property:** It is property of an element describing a linear relationship b/w the i/p & o/p.

It is the combination of two laws:

(i) law of Homogeneity.

(ii) law of Additivity.

Ex: $i(t) = 2V(t)$

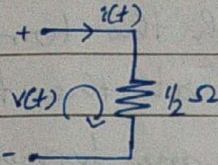

$$+V(t) - \frac{i(t)}{2} = 0 \Rightarrow i(t) = 2V(t). \quad \text{LOH: } V(t) \rightarrow S \rightarrow i(t) = 2V(t)$$

$$\downarrow \times a$$

$$i(t) = 2aV(t)$$

$$V(t) \xrightarrow{\times a} aV(t) \rightarrow S \rightarrow 2aV(t) \text{ (same)}$$

$$\text{LOA: } V_1(t) \rightarrow S \rightarrow i_1(t) = 2V_1(t). \quad + = 2V_1(t) + 2V_2(t)$$

$$V_2(t) \rightarrow S \rightarrow i_2(t) = 2V_2(t)$$

$$V_1(t) + V_2(t) \rightarrow S \rightarrow i'(t) = 2V_1(t) + 2V_2(t)$$

The system is linear.

- **Superposition theorem:** The voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or current through) that element due to each independent source acting alone.

Turned off: It means all the independent sources are replaced by their internal resistances. i.e we replace every voltage source by 0V, and every current source by 0A.

→ The dependent sources are left as they are.

→ The superposition theorem is not valid in case of non-linear circuits.

- **Thevenin's theorem:** A linear and bidirectional two terminal n/w can be replaced by an equivalent n/w consisting of a voltage source V_{TH} connected in series with a resistor R_{TH} .
 V_{TH} - open ckt voltage at the terminals.

R_{TH} : Input/Equivalent resistance at the terminals when the independent sources are turned off.

3. **Norton's theorem**: A linear and bidirectional two-terminal n/w can be replaced by an equivalent circuit consisting of a current source I_N in parallel with a resistor R_N .

I_N : Short ckt current through the terminals.

R_N : Input/Equivalent resistance at the terminals when the independent sources are turned off.

$$R_N = R_{TH}$$

$$I_N = \frac{V_{TH}}{R_{TH}}, \quad R_{TH} = \frac{V_{TH}}{I_N} \Rightarrow R_{TH} = R_N = \frac{V_{TH}}{I_N}$$

Source trans

Source transformation called
Thevenin-Norton transformation.

4. **Reciprocity theorem**: In a linear bidirectional single source n/w the ratio of response to excitation remains the same even when the positions of response & excitation are interchanged.

① The ratio of response to excitation is either 0 or ∞ .

② Only one independent source is present in the ckt. No dependent source is present in the ckt.

- **Millman's theorem**: If n voltage source with voltage $E_1, E_2, E_3, \dots, E_n$ and internal resistance $R_1, R_2, R_3, \dots, R_n$ are connected in parallel then these voltage sources can be replaced by a single source E in series with resistance R .

$$I_N = E_1/R_1 + E_2/R_2 + \dots + E_n/R_n, \quad R_N = R_1 || R_2 || \dots || R_n$$

$$1/R_N = 1/R_1 + 1/R_2 + \dots + 1/R_n$$

$$E = \frac{\sum_{i=1}^n E_i G_i}{\sum_{i=1}^n G_i}, \quad R = R_N$$

$$I = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + \dots + R_n}$$


$$I = \frac{\sum_{i=1}^n I_i R_i}{\sum_{i=1}^n R_i}$$

$$R = R_1 + R_2 + \dots + R_n$$

$$R = \sum_{i=1}^n R_i$$

Maximum Power Transfer theorem for DC circuits:

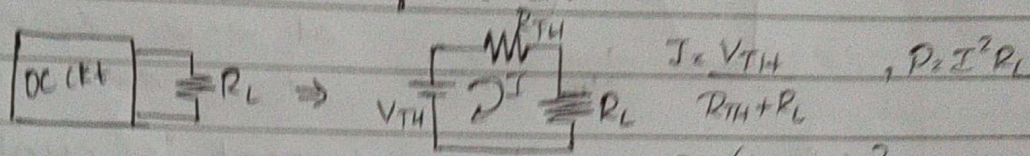Maximum power will be transferred to the load when the value of load resistance is equal to the Thevenin's equivalent resistance of the ckt.



$$P = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

$$\frac{dP}{dR_L} = 0 \Rightarrow \frac{dP}{dR_L} = \frac{V_{TH}^2 [(R_{TH} + R_L)^2 - 2R_L(R_L + R_{TH})]}{(R_{TH} + R_L)^4} = 0$$

$[R_L = R_{TH}]$ where maximum amount of power to load resistance.

- Compensation Theorem: If the resistance of any branch of a N/w is changed from R to $(R + \Delta R)$ where the current was originally I , then the change of current at any point in the n/w may be calculated by assuming that an e.m.f. $-I\Delta R$ has been introduced into the modified branch while all other sources have their e.m.f.'s suppressed and are represented by their internal resistances only.

Application: ① This theorem is useful to calculate the sensitivity of electrical n/w and bridges.

② It is useful in potentiometer ckt.

- Tellegen's Theorem: States if we have n elements in a ckt and the instantaneous voltage the elements are V_1, V_2, \dots, V_n and they will satisfy KVL.


and instantaneous current which obeys X_L

$$\varepsilon P = 0$$

$$\varepsilon P_{\text{supplied}} = \varepsilon P_{\text{absorbed}}, P = I^2 R = \frac{V^2}{R}$$

• Series Resonance in R-L-C circuits:

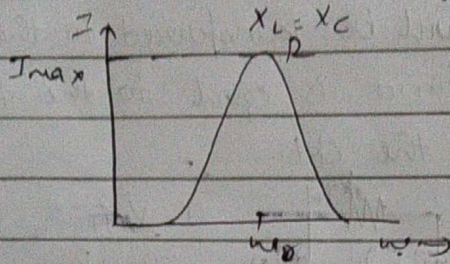Resonance: It is phenomenon at which the response of the ckt is max. for a particular frequency.



$$X_L = \omega L$$

$$X_C = 1/\omega C$$

$$\text{at } \omega = 0, X_C = \infty$$

$$\text{at } \omega = \infty, X_L = \infty$$

• At lower end the current is minimum.

At upper end the current is maximum, $X_L = X_C$

It is used in radio communication for selecting channel.

$$Q = 2\pi \times \frac{\text{Maximum Energy stored}}{\text{Energy dissipated}}$$

Bandwidth = The difference b/w half power freq.

$$B.W = f_2 - f_1 = \omega_2 - \omega_1, f = \frac{1}{2\pi\sqrt{LC}}$$

Impedance $\Rightarrow Z = R$ (Minimum)

Bandwidth $\Rightarrow BW = R/L$

Q.F $\Rightarrow Q = \omega L/R = 1/\omega CR$

Resonant Frequency $\Rightarrow \omega = 1/\sqrt{LC}$


$I = V/R$ (maximum)


• ~~Self~~ Resonance in Parallel R-L-C circuit.

$X_L = X_C$, Voltage & current are in phase

Impedance is max.

Current is Minimum.

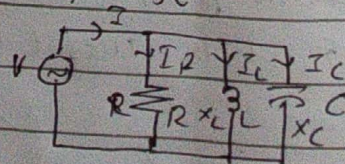

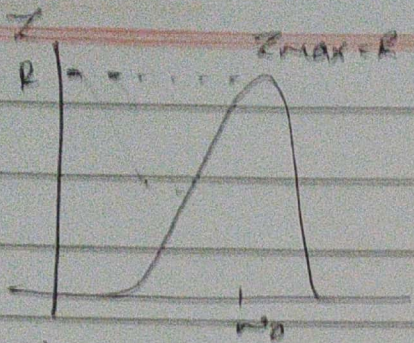

$$\omega = 0 \Rightarrow X_L = 0$$

$$\omega = \infty \Rightarrow X_C = 1/\omega C = 0$$

$$Z_{\max} = R$$

At $Z = R$ (Maximum)

Impedance

Bandwidth

$$BW = 1/RC$$

Q.F

$$Q = \omega RC$$

Resonant frequency

$$\omega = 1/\sqrt{LC}$$

Current

$$I = V/R \text{ (Maximum)}$$

- Python: Scrape Real Estate property.
Data from the web.
- Learnt about scraped website data - how the o/p will look like.
- Learnt about leading the webpage in python.
- How to Extracting div Tags.
- Extracting addresses and property details.
- Extracting Elements without unique identities.
- Saving the Extracted Data in csv files.
- Traveling through webpage.